



United International University

School of Science and Engineering

Quiz#05; Year 2020; Semester: Fall

Course: PHY 105; Title: Physics

Full Marks: 20; Section: A; Time: 20 minutes

Name:	ID:	Date:
--------------	------------	--------------

1. What is conductivity? What is the difference between resistivity and conductivity? **1**

2. What is surface charge density? What is its unit? **0.5**

3. A battery is known to have an emf of 9 volts. If a $7.9\ \Omega$ resistor is connected to the battery, the internal resistance is measured to be $3.7\ \Omega$. What is the terminal voltage of the battery? **2.5**

4. A 7.00 m length copper wire in a home has a diameter of 6 mm and carries a current of 13mA. The electric field inside in the wire is found as $3.75 \times 10^{-2}\text{ V/m}$. Calculate the resistivity of the copper wire. **2.5**

5. Find out the nominal, maximum and minimum resistance of the following resistor? **1**



6. Find the currents (i) I_1 ($10\ \Omega$), I_2 and I_3 ($8\ \Omega$) and the voltage V_x across $5\ \Omega$, and (ii) terminal voltage of the battery in the circuit shown below. **2.5**

