

Experiment No: 05

Name of Experiment: To investigate the characteristics of a series DC circuit and a parallel DC circuit and to verify Kirchhoff's Voltage Law (KVL) and to verify Kirchhoff's Current Law (KCL).

Data Sheet:

Table 3.1:

Nominal values of Resistance (Ω)	Measured values of Resistance by Ohmmeter (Ω)	Equivalent Resistance, R_T		Measured voltage across each resistor (V)	Calculated Voltage using VDR (V)
		Measured R_T by using Ohmmeter(Ω)	Calculated $R_T = R_1 + R_2 + R_3$ (Ω)		
$R_1 = 50$	52.5	250	50+90+115=255	$V_1 = 7.84$	7.843
$R_2 = 90$	94.5			$V_2 = 14.12$	14.118
$R_3 = 115$	120.75			$V_3 = 18.04$	18.039

Calculation:

$$I = \frac{V_s}{R_T} = \frac{40}{255} = 0.15686 = 0.16 \text{ A.}$$

$$R_1 = V_1 / 0.16 = 7.84 / 0.16 = 49 \text{ ohm}$$

$$R_2 = V_2 / 0.16 = 14.12 / 0.16 = 88.25 \text{ ohm}$$

$$R_3 = V_3 / 0.16 = 18.04 / 0.16 = 112.75 \text{ ohm}$$

Therefore,

$$\text{Sum of } R_T \text{ (by using ohmmeter)} = 49 + 88.25 + 112.75 = 250 \Omega$$

Here, $V_s = 40 \text{ volt}$

$$V_1 = (R_1 / R_T) \times V_s = (50 / 255) \times 40 = 7.843 \text{ Volt}$$

$$V_2 = (R_2 / R_T) \times V_s = (90 / 255) \times 40 = 14.118 \text{ Volt}$$

$$V_3 = (R_3 / R_T) \times V_s = (115 / 255) \times 40 = 18.039 \text{ Volt}$$

Therefore,

$$\text{Sum of } V_L = 7.843 + 14.118 + 18.039 = 40 \text{ volt}$$

According to KVL,

$$V_{\text{gain}} = V_{\text{lost}}$$

$$V_{\text{gain}} = V_s = 40 \text{ Volt (Theoretical value)}$$

$$V_{\text{lost}} = V_L = 7.843 + 14.118 + 18.039 = 40 \text{ Volt (Experimental value)}$$

$$\% \text{Error: } \frac{|40 - 40|}{40} \times 100\% = 0\%$$

$$\text{Accuracy: } (100\% - \% \text{Error}) = 100\% - 0\% = 100\%.$$

Now,

$$R_T \text{ (by using ohmmeter)} = 250 \, \Omega$$

$$\text{Theoretical, } R_T = 255 \, \Omega$$

$$\% \text{Error: } \frac{|255-250|}{255} \times 100\% = 1.96\%$$

$$\text{Accuracy: } (100\% - \% \text{Error}) = 100\% - 1.96\% = 98.04\%.$$

Assignment:

What can you deduce about the characteristics of a series Circuit from observation Table 3.1?

Answer:

Series circuit is a circuit where two or many resistances are placed accordingly at a particular line. In figure 3.1, we can see such a circuit. From Table 3.1, we can notice that R_T is the sum of all the three resistors. We can observe information from that table that relates to the characteristics of a series circuit. We know in series circuit the voltages per resistances are not same. They are always different.

From the data found in Table 3.1, mathematically prove that the current in the series network of figure 3.3 is equal for each resistance.

Answer:

In figure 3.3,

$$R_1 = 50\Omega, R_2 = 90 \, \Omega, R_3 = 115 \, \Omega$$

From the Table 3.1,

$$V_1 = 7.84 \text{ Volt}, V_2 = 14.12 \text{ Volt}, V_3 = 18.04 \text{ Volt}$$

$$I_1 = 0.15684 = 0.16 \text{ A},$$

$$I_2 = 0.156821 = 0.16 \text{ A},$$

$$I_3 = 0.15686 = 0.16 \text{ A}.$$

Therefore,

$$I_1 = I_2 = I_3 \text{ (Verified).}$$

Verify KVL from the data obtained in Table 3.1.

Answer:

From Table 3.1,

$$V_s = 40 \text{ Volt}$$

$$I = \frac{V_s}{R_T} = \frac{40}{250} = 0.16 \text{ A.}$$

$$V_1 = IR_1 = 7.84 \text{ volt}$$

$$V_2 = IR_2 = 14.12 \text{ volt}$$

$$V_3 = IR_3 = 18.04 \text{ volt}$$

$$V_s + (-IR_1) + (-IR_2) + (-IR_3) = 0$$

$$\rightarrow 40 - 7.84 - 14.12 - 18.04 = 0$$

$$\therefore \sum v = 0 \text{ (KVL verified)}$$

Data Sheet:

Table 4.1:

Nominal values of Resistance (Ω)	Measured values of Resistance by Ohmmeter (Ω)	Equivalent Resistance, R_T		Measured current through each resistor (A)	Calculated Current using CDR (A)
		Measured R_T by using Ohmmeter(Ω)	Calculated $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \text{ (}\Omega\text{)}$		
$R_1 = 40$	42	21.127	21.086	$I_1 = 0.75$	0.749
$R_2 = 75$	48.75			$I_2 = 0.40$	0.399
$R_3 = 110$	115.05			$I_3 = 0.27$	0.272

Calculation:

$$V_s = 30 \text{ Volt}$$

$$R_1 = \frac{v}{I_1} = \frac{30}{0.75} = 40 \text{ ohm}$$

$$R_2 = \frac{v}{I_2} = \frac{30}{0.40} = 75 \text{ ohm}$$

$$R_3 = \frac{v}{I_3} = \frac{30}{0.27} = 111.11 \text{ ohm}$$

Therefore,

$$\text{Sum of } R_T \text{ (by using ohmmeter)} = 21.127 \text{ ohm}$$

$$I_T = 0.75 + 0.40 + 0.27 = 1.42 \text{ A.}$$

$$I_1 = (R_T/R_1) \times I_T = (21.086/40) \times 1.42 = 0.749 \text{ A}$$

$$I_2 = (R_T/R_2) \times I_T = (21.086/75) \times 1.42 = 0.399 \text{ A}$$

$$I_3 = (R_T/R_3) \times I_T = (21.086/110) \times 1.42 = 0.272 \text{ A}$$

Therefore,

$$\text{Sum of } I_L = 0.749 + 0.399 + 0.272 = 1.42 \text{ A}$$

According to KCL,

$$I_{in} = I_{out}$$

$$I_{in} = I_T = 1.42 \text{ A}$$

$$I_{out} = I_L = I_1 + I_2 + I_3 = 0.749 + 0.399 + 0.272 = 1.42 \text{ A}$$

$$\% \text{Error: } \frac{|1.42 - 1.42|}{1.42} \times 100\% = 0\%$$

$$\text{Accuracy: } (100\% - \% \text{Error}) = 100\% - 0\% = 100\%.$$

Now,

$$R_T (\text{experimental}) = 21.127 \Omega$$

$$R_T (\text{theoretical}) = 21.086 \Omega$$

$$\% \text{Error: } \frac{|21.127 - 21.086|}{21.086} \times 100\% = 0.194\%$$

$$\text{Accuracy: } (100\% - \% \text{Error}) = 100\% - 0.194\% = 99.806\%.$$

Assignment:

What can you deduce about the characteristics of a parallel circuit from observation Table 4.1?

Answer:

Parallel circuits are arranged such that current can Travel through different branches simultaneously. In figure 4.4, we can see such a circuit. From Table 4.1, we can notice that $\frac{1}{R_T}$ is the sum of all the three Resistors. We can observe information from that table that relates to the characteristics of a parallel circuit. Here, the voltage remains constant in every resistance.

From the data found in Table 4.1, Calculate I_1 , I_2 and I_3 using Ohm's Law.

Answer:

From Table 4.1,

$$R_1 = 40 \Omega, R_2 = 75 \Omega, R_3 = 110 \Omega, V_s = 30 \text{ Volt}$$

Using Ohm's Law,

$$I_1 = V / R_1 = 30 / 40 = 0.75 \text{ A}$$

$$I_2 = V / R_2 = 30 / 75 = 0.40 \text{ A}$$

$$I_3 = V / R_3 = 30 / 110 = 0.27 \text{ A}$$

Verify KCL from the data obtained in Table 4.1.

Answer:

From Table 4.1,

$$I_{in} = I_{out}$$

$$I_{in} = I_T = 1.42 \text{ A}$$

$$I_{out} = I_1 + I_2 + I_3 = 0.749 + 0.399 + 0.272 = 1.42 \text{ A}$$

$$I_T - (I_1 + I_2 + I_3) = 0$$

$$\rightarrow 1.42 - (0.749 + 0.399 + 0.272) = 0$$

$$\therefore \sum I = 0 \text{ (KCL verified)}$$

Azizul Islam Nayem. PHY 2106. Section D. 011201262 .