



United International University

School of Science and Engineering

Quiz#05; Year 2020; Semester: Fall

Course: PHY 105; Title: Physics

Full Marks: 20; Section: E; Time: 20 minutes

Name:	ID:	Date:
--------------	------------	--------------


1. What is emf? What is the difference between DC and AC Current? 1

2. What is current density? What is its unit? 0.5

3. A $45\ \Omega$ resistor is connected to the terminals of a battery whose emf is 9 V and whose internal resistance is $2.5\ \Omega$. Calculate (a) the current in the circuit, (b) the terminal voltage of the battery, and (c) the power dissipated in the resistor R and in the battery's internal resistance r . 2.5

4. A 4.00 m length copper wire in a home has a diameter of 2 mm and carries a current of 10 mA . The drift speed of the electrons is found as $3.75 \times 10^{-6}\text{ m/s}$. Calculate the conduction electron density in copper wire. [Given, $e = 1.6 \times 10^{-19}\text{ C}$] 2.5

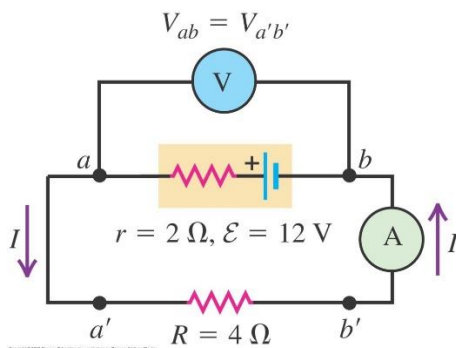5. What are voltmeter and ammeter readings in the following ckt? 1



6. Find the currents I , I_1 , I_2 and I_3 and the voltage V_x across $35\ \Omega$ in the circuit shown below. 2.5

